


VHDL

System Design Principles

©Hanan Ribo

High Level System Description




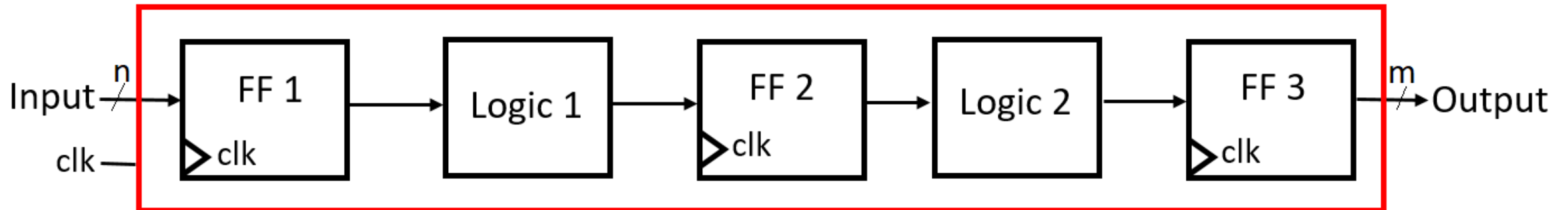
- The most common mistake is to start HDL coding before describing the required digital system in high level of RTL form.
- In RTL system description it becomes clear what are the system's combinational and synchronous subunits.
- Any digital logic system can be disassembled to logic blocks chained to FFs (registers) .




System separation to combinational and synchronous subunits

There are four building blocks of combinational and synchronous subunits:

 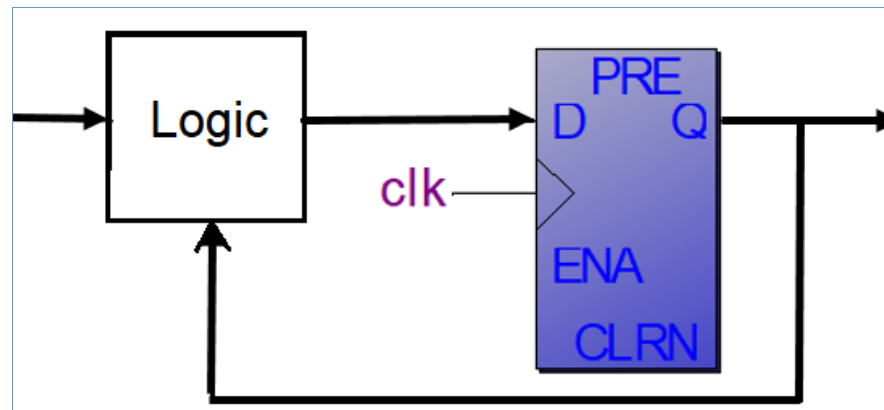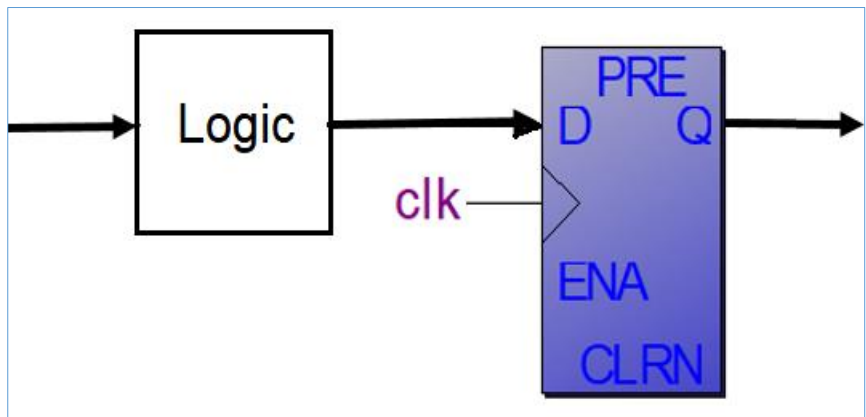 1. Pure logic
2. Pure synchronous (single **or** multiple chained)
3. Logic through Synchronous
4. Logic through Synchronous feedback




Example of Digital System Disassembly

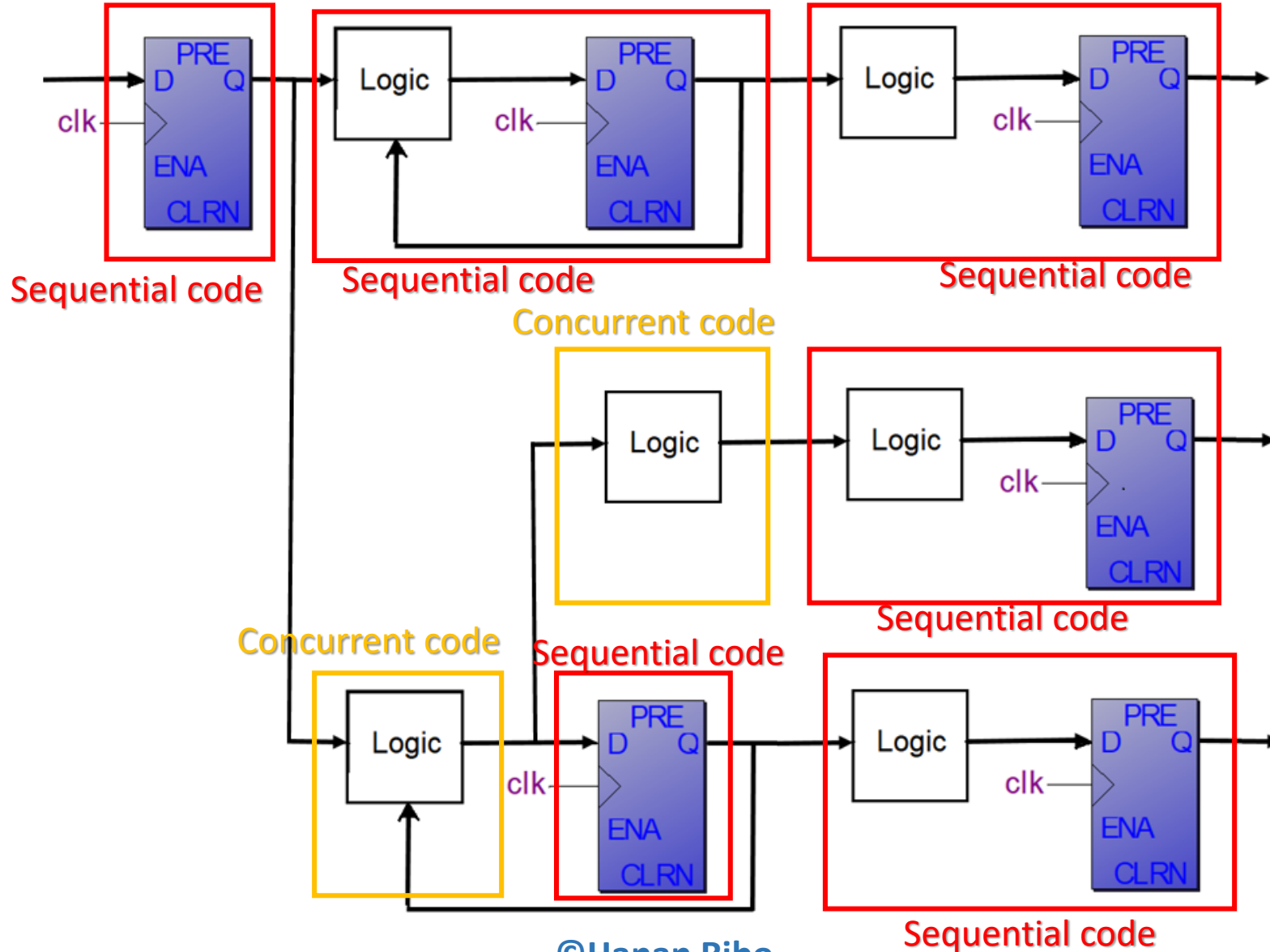

Mixed Process

- Mixed PROCESS is a PROCESS which combines combinatorial and synchronous elements inside it (even Latch elements).
- Don't write Mixed PROCESS, is non synthesizable (ieee-1076.6 standard).
- When you write a PROCESS, ask yourself if it describes combinatorial logic **or** synchronous circuit. If you're not sure, you are writing a Mixed PROCESS.
- Synchronous derivator example – circuit implementation:

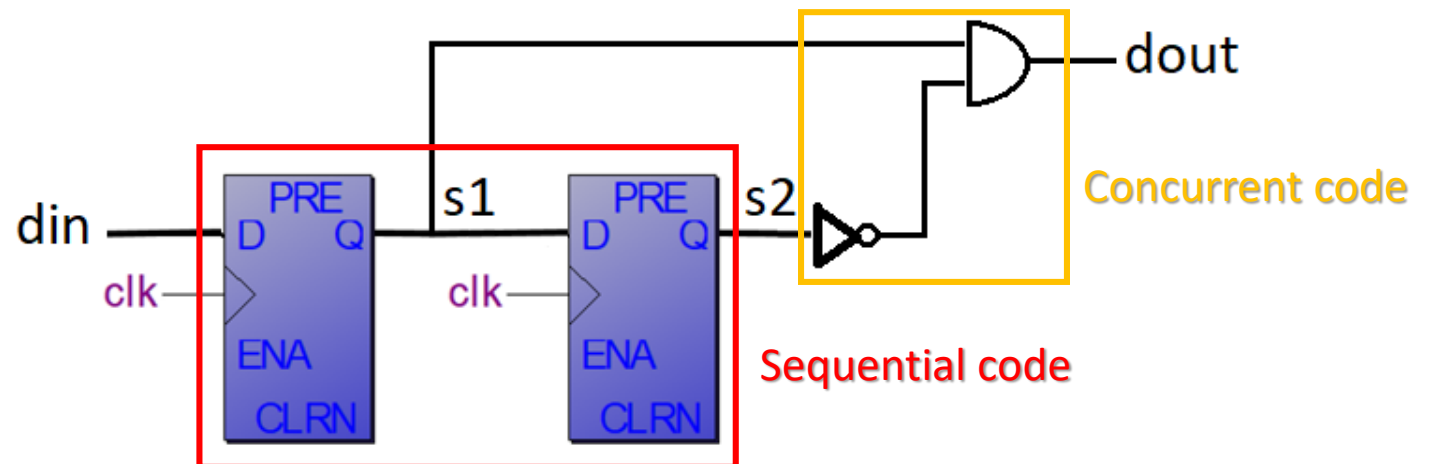Note: without dismantle it into two parts, you write a Mixed PROCESS



Mixed Process – Synchronous derivator


```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```

```
-----  
entity deriv is  
  port(  
    clk : in std_logic;  
    din : in std_logic;  
    dout : out std_logic  
  );  
end deriv;
```

```
-----  
architecture rtl of deriv is  
  signal s1,s2 : std_logic;  
begin
```

```
  process (clk,s1,s2)  
  begin  
    if (clk'event and clk='1') then  
      s1 <= din;  
      s2 <= s1;  
    end if;  
    dout <= s1 and not s2;  
  end process;
```

```
end rtl;
```

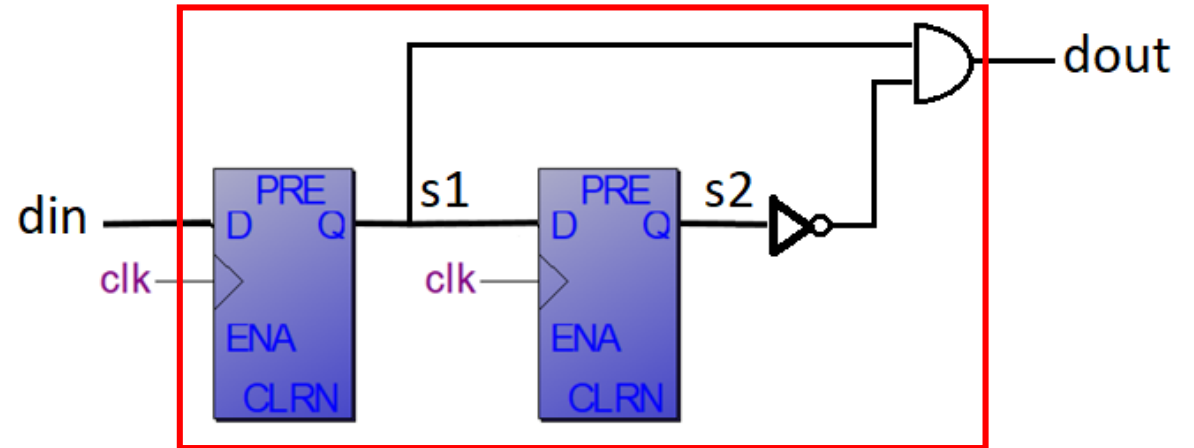

The PROCESS combines
combinatorial and synchronous
elements inside it

Synchronous derivator – correct approach

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```


```
-----  
entity deriv is  
  port(  
    clk : in std_logic;  
    din : in std_logic;  
    dout : out std_logic  
  );  
end deriv;
```

```
-----  
architecture rtl of deriv is  
  signal s1,s2 : std_logic;  
begin
```

```
  process(clk)  
  begin  
    if (clk'event and clk='1') then  
      s1 <= din;  
      s2 <= s1;  
    end if;  
  end process;
```

```
  dout <= s1 and not s2;
```

```
end rtl;
```

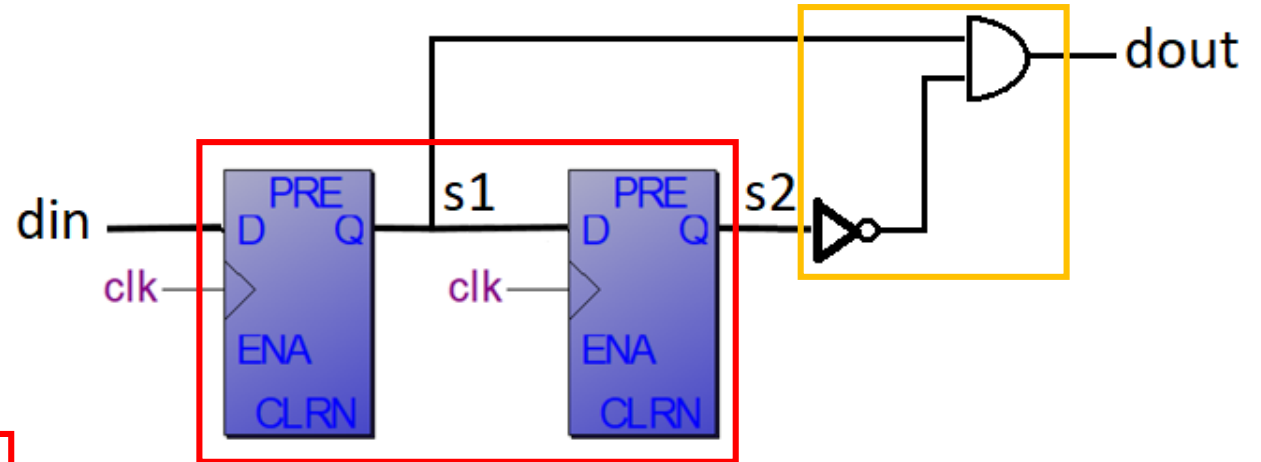


Sequential code

Concurrent code

Question:


How to implement the given circuit ?

Option No.1

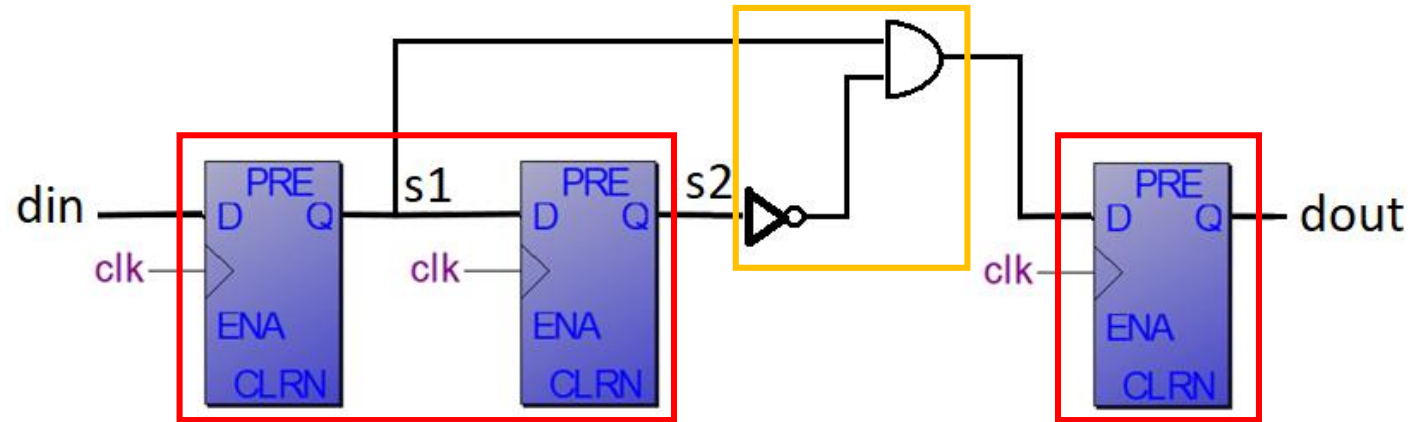

Correct but
contains
redundancy

Option No.2

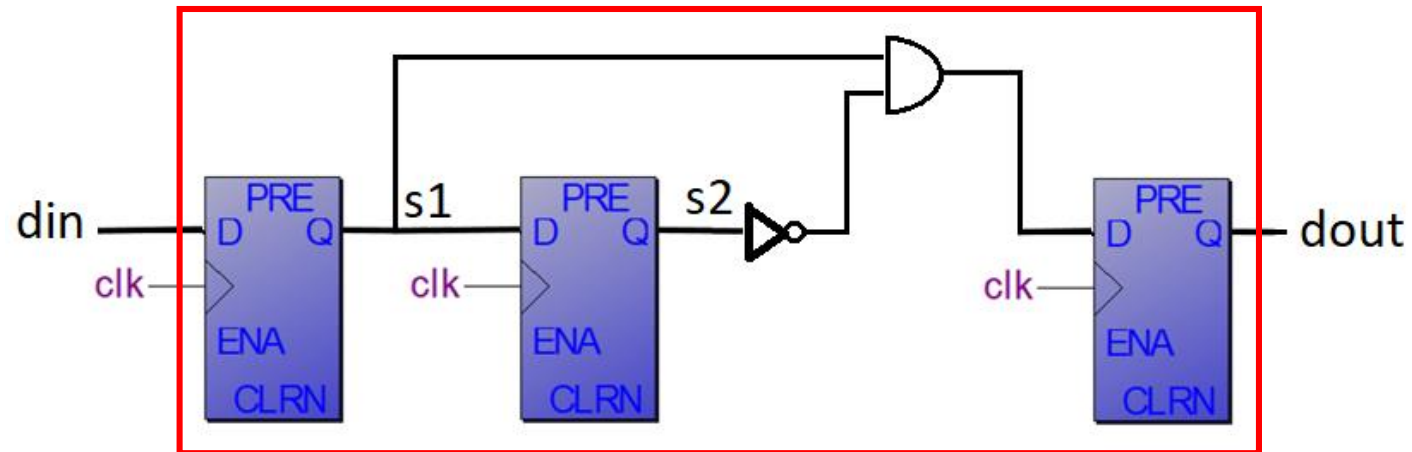

Correct: Pure
synchronous
(multiple
chained)

Pure synchronous (multiple chained) PROCESS


```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```

```
-----  
entity deriv is  
  port(  
    clk : in std_logic;  
    din : in std_logic;  
    dout : out std_logic  
  );  
end deriv;
```

```
-----  
architecture rtl of deriv is  
  signal s1,s2 : std_logic;  
begin
```

```
  process (clk)  
  begin  
    if (clk'event and clk='1') then  
      s1 <= din;  
      s2 <= s1;  
      dout <= s1 and not s2;  
    end if;  
  end process;
```

```
end rtl;
```

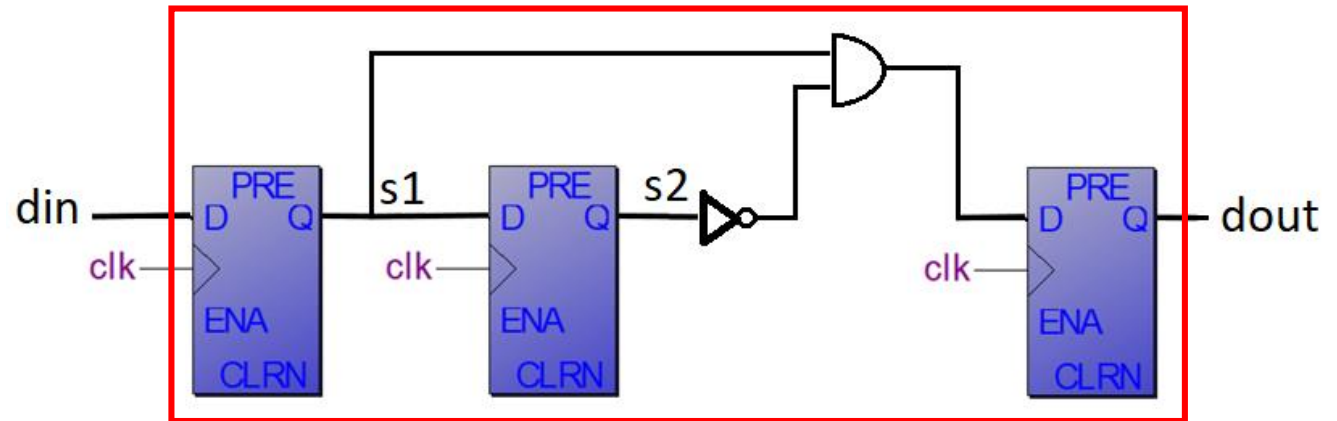

Sequential code