

VHDL - Combinatorial PROCESS Logic Synthesis

©Hanan Ribo

Introduction

- The next step after HDL code Simulation is HDL code Synthesis.
- Synthesis contains the next three steps:
 - ✓ conversion of the high-level VHDL (or Verilog) language, which describes the circuit at the Register Transfer Level (RTL), into a netlist at the gate level.
 - ✓ Optimization of the gate-level netlist for speed (minimize critical path) and for area (minimize Logic function).
 - ✓ Implementation of the optimized gate-level netlist based on **MUXs+LUTs, Latches, FFs** (in case of FPGA as a target Hardware).
- The last step is a place and route (fitter), software will generate the physical layout for a FPGA chip or will generate the masks for an ASIC chip.

Synthesis coding approach

- Synthesis tools and Simulation tools translate PROCESS based HDL code in a different way (concurrent code translated in the same way).
- Synthesis tools search for adjustment of VHDL code to one of the next three template kinds (*ieee-1076.6 standard*):
Combinational Logic, Synchronous Logic, Latch based Logic.
- Our goal:
 - ✓ writing of HDL code which will be translated in the same exact way by all Synthesis and Simulation tools.
 - ✓ Avoid of HDL code which synthesized with hardware errors in the required design (**must avoid from Sick Hardware**).
 - ✓ **Important rule: when you write HDL code, think Hardware!**

Note: Unusual and Unsupported design approach

With a guarded BLOCK or with WHEN statements (using concurrent code) even very simple sequential circuits can be constructed. This, however, is Unusual and Unsupported design approach.

In conclusion: Synchronous design will be described using PROCESS only!

DFF implementation example using concurrent code

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

-----

ENTITY dff IS
    PORT ( d, clk, rst: IN STD_LOGIC;
          q: OUT STD_LOGIC);
END dff;

-----

ARCHITECTURE dff OF dff IS
BEGIN
    b1: BLOCK (clk'EVENT AND clk='1')
    BEGIN
        q <= GUARDED '0' WHEN rst='1' ELSE d;
    END BLOCK b1;
END dff;
```

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

-----

ENTITY dff IS
    PORT ( d, clk : IN STD_LOGIC;
          q : BUFFER STD_LOGIC);
END dff;

-----

ARCHITECTURE dff OF dff IS
BEGIN
    q <= d WHEN clk'event and clk='1' ELSE q;
END dff;
```

PROCESS Logic Synthesis

The way we write a PROCESS affects its synthesis and is associated with one of the following two synthesis types:

- **Combinatorial PROCESS (Combinational Logic Circuit):**

- ✓ PROCESS that its sensitivity list contains all its internal input SIGNALS and the PROCESS doesn't contain IF-THEN statement which its condition on SIGNAL event.
- ✓ This kind of PROCESS describes a combinational logic circuit.
- ✓ If we write a partial sensitivity list, the compiler completes it, differ from simulation environment.

- **Sequential PROCESS (Synchronous / Asynchronous Logic Circuit):**

- ✓ PROCESS that its sensitivity list contains a input SIGNAL and the PROCESS contains IF-THEN statement which its condition on SIGNAL event.
- ✓ This kind of PROCESS describes FFs based sequential logic circuit triggered by a SIGNAL event.

Combinatorial PROCESS - Rules

In order the compiler will synthesize the a PROCESS as a Combinational Logic Circuit we must obey the next three rules (Combinational Logic template):

Rule 1: Make sure that all the input SIGNALS of the required combinational circuit appear in the PROCESS sensitivity list.


Rule 2: Don't use IF-THEN statement which its condition on SIGNAL event (SIGNAL transition).

Rule 3: PROCESS must cover all the permutations (full truth table description) of the input and output SIGNALS of the combinational circuit.

- ✓ Use ELSE option in IF-THEN statement.
- ✓ For a complex Combinational Circuit description, use default SIGNALS assignments (at the PROCESS beginning we write all the default output SIGNALS assignment and later we use IF-THEN without covering all permutations).

General rules for Combinational Logic Circuit

 - **General Rule 1:** Use SIGNALS assignment without feedback (a SIGNAL must appear only in one assignment side).
- **General Rule 2:** Avoid from multiple assignment to the same SIGNAL from different PROCESSES (cause multiple driven).



Combinatorial PROCESS – MUX 3-1 example

- The PROCESS must cover all the permutations (full truth table description) of the input and output SIGNALS of the combinational circuit.

```
entity mux is port(  
    I0, I1, I2 : in std_logic_vector(2 downto 0);  
    S : in std_logic_vector(1 downto 0);  
    O : out std_logic_vector(2 downto 0));  
end mux;
```


- **Attitude 1**: use ELSE option in IF-THEN statement.
- **Attitude 2**: use default SIGNALS assignments

```
architecture rtl of mux is  
begin  
    process(I2,I1,I0,S)  
    begin  
        if      S = "00" then O <= I0;  
        elsif  S = "01" then O <= I1;  
        else  
            O <= I2;  
        end if;  
    end process;  
end rtl;
```

```
architecture rtl of mux is  
begin  
    PROCESS (I2, I1, I0, S)  
    BEGIN  
        O <= I2 ;  
        IF      S="00" THEN O <= I0 ;  
        ELSIF  S="01" THEN O <= I1 ;  
        END IF;  
    END PROCESS ;  
end architecture rtl;
```


Combinatorial PROCESS – MUX 3-1 example

Synthesis result:

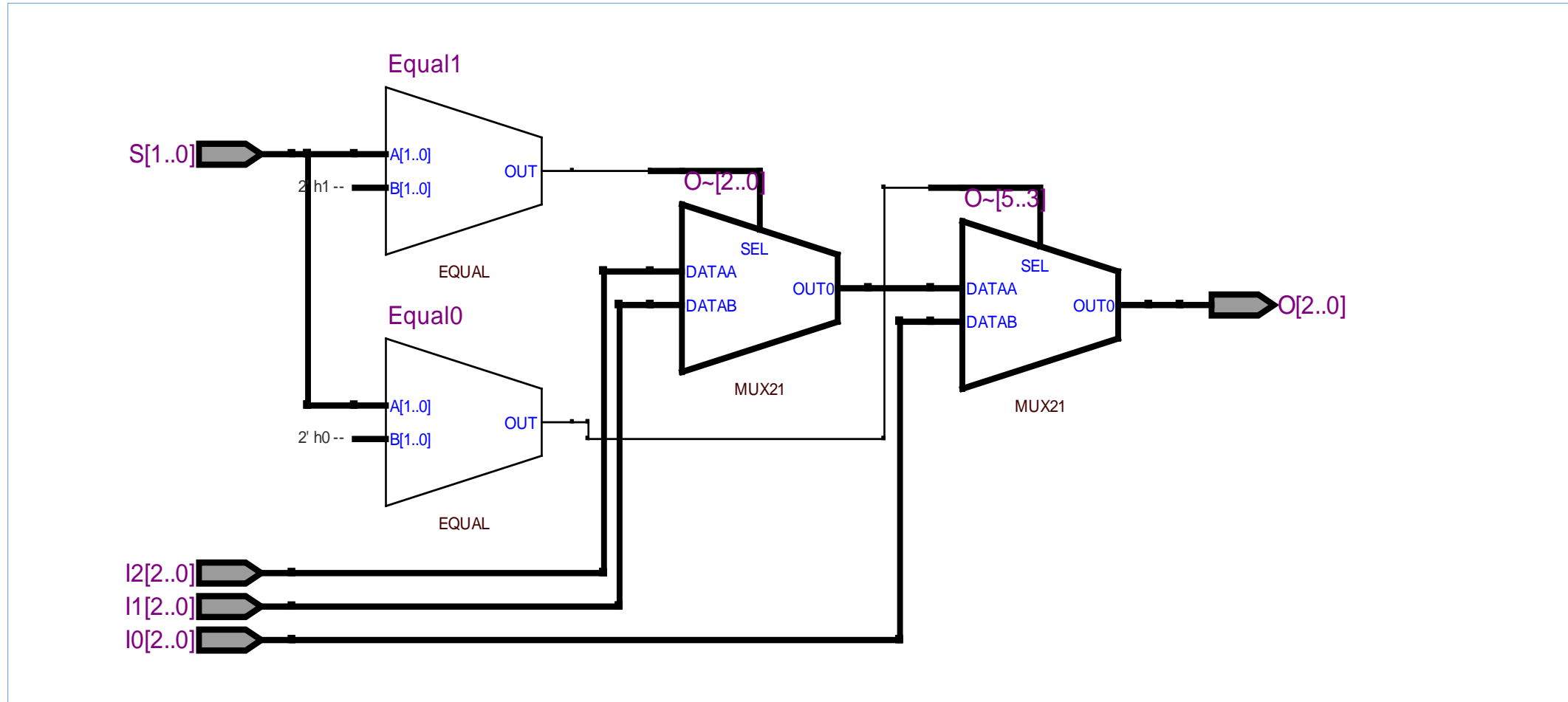

Wrong Combinatorial PROCESS (Sick HW)


- The next PROCESS doesn't cover all the input S permutations of the combinational circuit (permutation S="11" is missing, in order to hold the output O last value, tree Latches will be inferred) .

```
entity mux is port(  
    I0, I1, I2 : in std_logic_vector(2 downto 0);  
    S : in std_logic_vector(1 downto 0);  
    O : out std_logic_vector(2 downto 0));  
end mux;
```

```
architecture rtl of mux is  
begin  
    process(I2, I1, I0, S)  
    begin  
        if S = "00" then O <= I0;  
        elsif S = "01" then O <= I1;  
        elsif S = "10" then O <= I2;  
        end if;  
    end process;  
end rtl;
```

Wrong Combinatorial PROCESS (Sick HW)

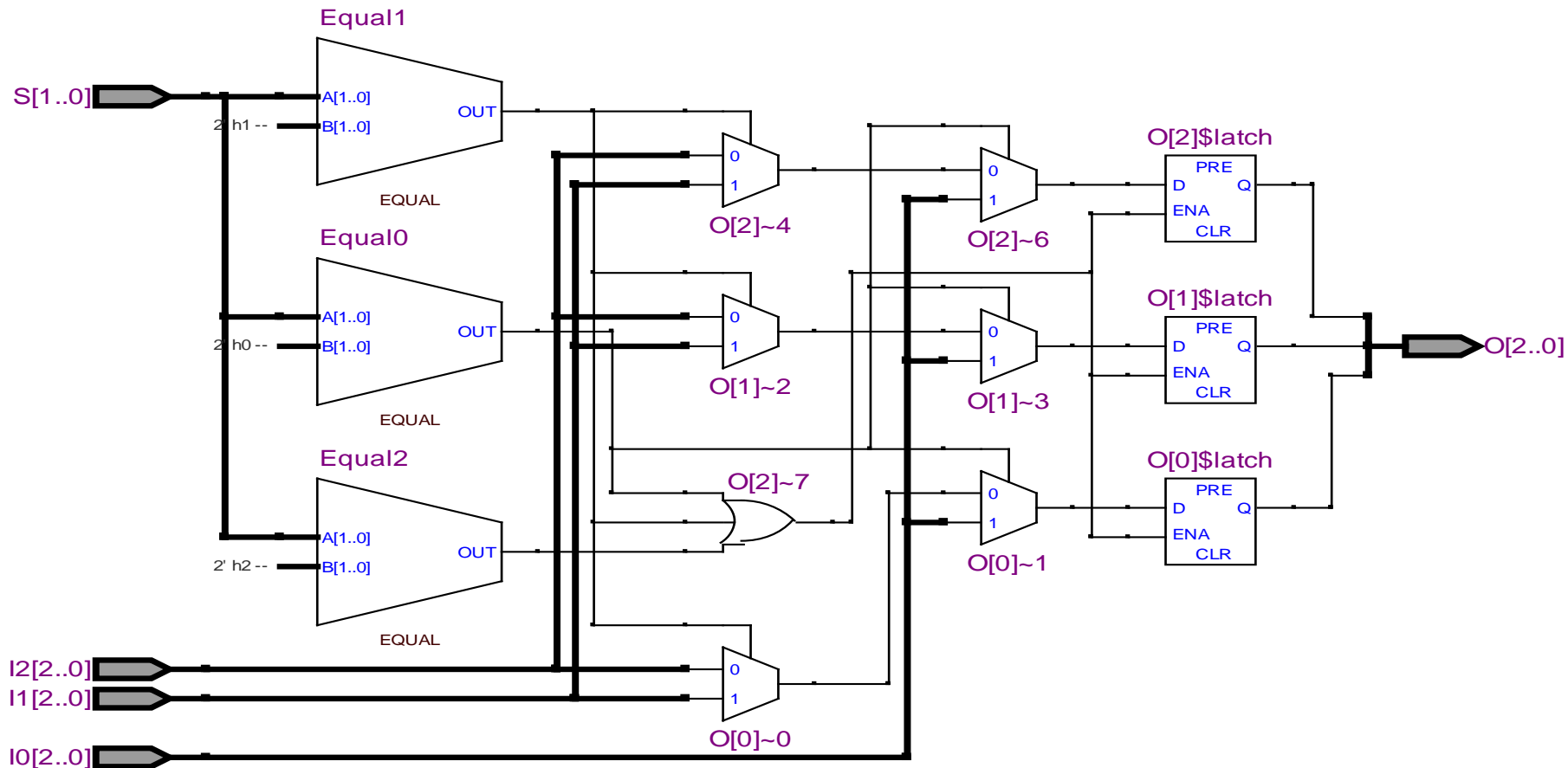Synthesis result (we meant for MUX 3-1, the result is a Sick HW):



Simulation vs Synthesis



case3 code
simulation
doesn't
describe
AND gate

Don't use **SIGNALS** for
Intermediate calculations

```
library ieee;  
use ieee.std_logic_1164.all;  
use IEEE.std_logic_unsigned.all;  
use ieee.std_logic_arith.all;  
-----  
entity case3 is port(  
    a,b : in std_logic;  
    y    : out std_logic);  
end case3;  
-----  
architecture arc of case3 is  
    signal c : std_logic;  
begin  
    process (a, b)  
    begin  
        c <= a and b ;  
        y <= c ;  
    end process ;  
end architecture arc;
```

Combinatorial PROCESS: The PROCESS covers all the permutations (full truth table description) of the input and output SIGNALS of the combinational circuit.

Synthesis result:

  

Wrong Combinatorial PROCESS (Sick HW)

```
entity selector is
  port(
    a,b,c,d : in std_logic;
    sel : in integer range 0 to 3;
    x,y : out std_logic
  );
end selector;
```

```
architecture arc of selector is
begin
```

```
  process (a,b,c,d,sel)
```

```
  begin
```

```
    if (sel=0) then
```

```
      x<=a;
```

```
      y<='0';
```

```
    elsif (sel=1) then
```

```
      x<=b;
```

```
      y<='1';
```

```
    elsif (sel=2) then
```

```
      x<=c;
```


```
    else
```

```
      x<=d;
```

```
    end if;
```


```
  end process;
```

```
end arc;
```

 


sel	x	y	sel	x	y
00	a	0	00	a	0
01	b	1	01	b	1
10	c		10	c	y
11	d		11	d	y

 the specifications provided for y are incomplete, as can be observed in the truth-table. Therefore, a latch will be implemented, which renders the previous y value.



Wrong Combinatorial PROCESS (Sick HW)

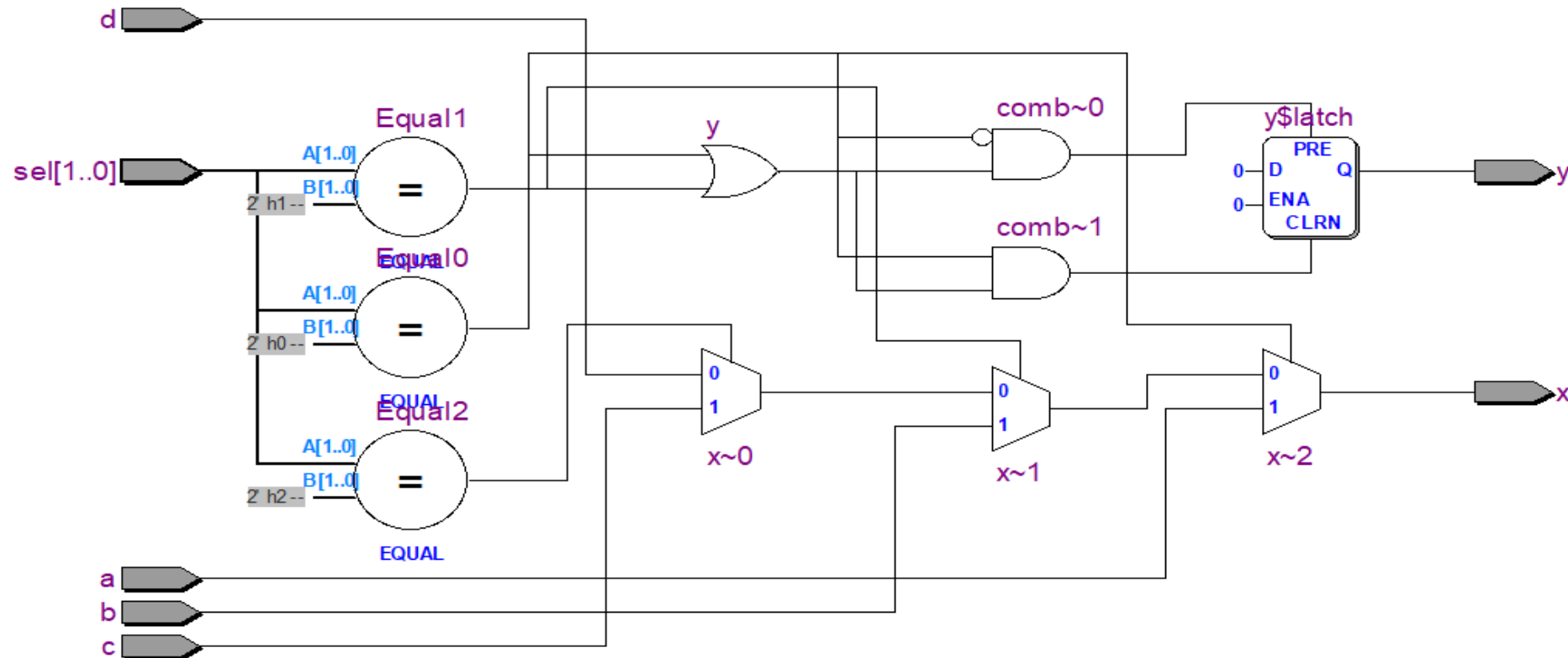Synthesis result (we meant for selector, the result is a Sick HW):



$y = 0$ when $CLR_N = 1$: $CLR_N = ((sel == 1) \text{ or } (sel == 0)) \text{ and } (sel == 0)$
 $y = 1$ when $PRESET = 1$: $PRESET = ((sel == 1) \text{ or } (sel == 0)) \text{ and not}((sel == 0))$
 $y = (sel(0) \text{ AND } sel(1)) \text{ OR } (sel(0) \text{ AND } y) \text{ OR } (sel(1) \text{ AND } y)$