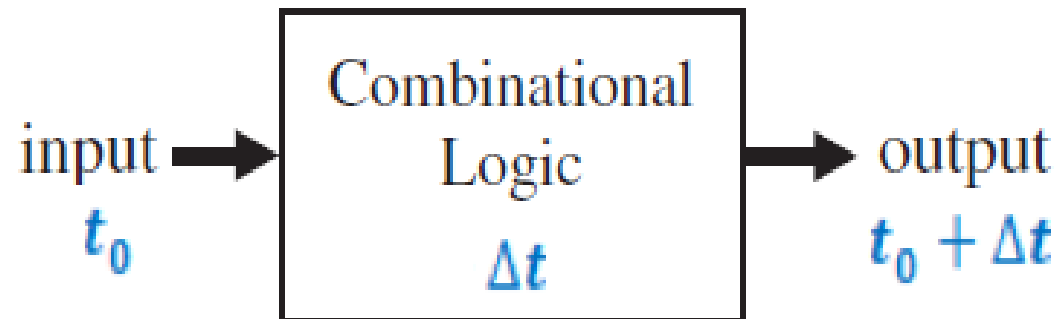


VHDL - Concurrent Code Dataflow modeling

©Hanan Ribo

Introduction

- VHDL code can be concurrent (combinational logic) or sequential (sequential logic).
- **Combinational logic - definition:**
The output is a pure function of the present input only (implemented by Boolean circuits, using conventional logic gates only – no memory, no feedback).
- Intuitively, the circuit information flows in parallel.




Introduction

- **Sequential logic - definition:**

The output does depend on present inputs and previous inputs (implemented using storage, flip-flops elements, which are connected to the combinational logic block through a feedback loop).

 
- Intuitively, the circuit information flows in serial triggered by clk signal.



Introduction

- **Note**: not any circuit that possesses storage elements is sequential.
- **Example**: RAM memory.

 The storage elements appear in a forward path rather than in a feedback loop. The memory-read operation depends only on the present address vector input (with nothing to do with previous memory accesses).



Introduction

- There are four types of **ARCHITECTURE** Modeling styles:
 - ✓ Dataflow modeling = Concurrent Code
 - ✓ Structural modeling = Concurrent Code
 - ✓ Behavioral modeling = Sequential Code
 - ✓ Mixed modeling = Concurrent Code

Concurrent code - Dataflow

- Concurrent code dataflow approach is based on four kind of statements that can only be used outside **PROCESSES**, **FUNCTIONS**, or **PROCEDURES** (Three sequential code mechanism).
 - ✓ Signal assignment using **Operators** (with no feedback)
 - ✓ The **WHEN** statement (two kinds - **WHEN/ELSE** or **WITH/SELECT/WHEN**)
 - ✓ The **GENERATE** statement
 - ✓ The **BLOCK** statement
- The order of concurrent statements doesn't matter, due to concurrent execution.
- [Notepad++ Download \(highly recommended\)](#)

Signal assignment-using Operators

- Using Operators is the most basic way of creating concurrent code. Operators can be used to implement any combinational circuit.

- Syntax:** `signal_name <= expression ;`


Operator type	Operators	Data types
Logical	NOT, AND, NAND, OR, NOR, XOR, XNOR	BIT, BIT_VECTOR, STD_LOGIC, STD_LOGIC_VECTOR, STD_ULOGIC, STD_ULOGIC_VECTOR
Arithmetic	+, -, *, /, ** (mod, rem, abs)	INTEGER, SIGNED, UNSIGNED
Comparison	=, /=, <, >, <=, >=	All above
Shift	sll, srl, sla, sra, rol, ror	BIT_VECTOR
Concatenation	&, (,,)	Same as for logical operators, plus SIGNED and UNSIGNED

- Note 1:** Signal assignment with feedback causes buffer inferred, in order to save the last signal value.

Signal assignment-using Operators


- **Note 2:** concurrent code must not use multiple driven assignments. Its implementation shortcuts Vcc to gnd.

```
Z <= not A;  
Z <= A or B;
```

 

 - **Example 1:**



```
qa <= r or t;  
qb <= (qa and not (g xor h)) ;
```



Signal assignment-using Operators (Mux 4-1)

  Example 2:

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
-----  
  
ENTITY mux IS  
    PORT ( a, b, c, d, s0, s1: IN STD_LOGIC;  
          y: OUT STD_LOGIC);  
  
END mux;  
  
-----  
  
ARCHITECTURE pureLogic OF mux IS  
BEGIN  
    y <= (a AND NOT s1 AND NOT s0) OR  
         (b AND NOT s1 AND s0) OR  
         (c AND s1 AND NOT s0) OR  
         (d AND s1 AND s0);  
  
END pureLogic;
```



Conditional signal assignment

- **Syntax:**


*Priority
Mux based
on 2-1 MUX
cascade*

```
signal_name <= assignment WHEN condition1 ELSE  
                    assignment WHEN condition2 ELSE  
                    .....  
                    .....  
                    assignment WHEN condition3 ELSE  
                    assignment ;
```

- **Note:** If **ELSE** is not required, this method should not be used.

 - **Example 1:**

```
q <= a WHEN sela = '1' ELSE  
    b WHEN selb = '1' ELSE  
    c ;
```



Conditional signal assignment (Mux 4-1)

- **Example 2:**


```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

-----

ENTITY mux IS
    PORT ( a, b, c, d: IN STD_LOGIC;
          sel: IN INTEGER RANGE 0 TO 3;
          y: OUT STD_LOGIC);
END mux;

-----

 ARCHITECTURE mux1 OF mux IS
BEGIN
    y <= a WHEN sel=0 ELSE
        b WHEN sel=1 ELSE
        c WHEN sel=2 ELSE
        d;
END mux1;
```



unaffected value using in WHEN statement

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

-----

ENTITY mux3_8 IS
    GENERIC (n : INTEGER := 8;
            k : integer := 3 -- k=log2(n)
            );


    PORT (MUXin:  IN STD_LOGIC_VECTOR (n-1 downto 0);
          sel:    IN STD_LOGIC_VECTOR (k-1 downto 0);
          MUXout: OUT STD_LOGIC);
END mux3_8;

-----

ARCHITECTURE rtl OF mux3_8 IS
BEGIN

    MUXout <= MUXin(0)  when sel = "000" else
              MUXin(1)  when sel = "001" else
              MUXin(2)  when sel = "010" else
              MUXin(3)  when sel = "011" else
              unaffected ; -- when other options


END rtl;
```

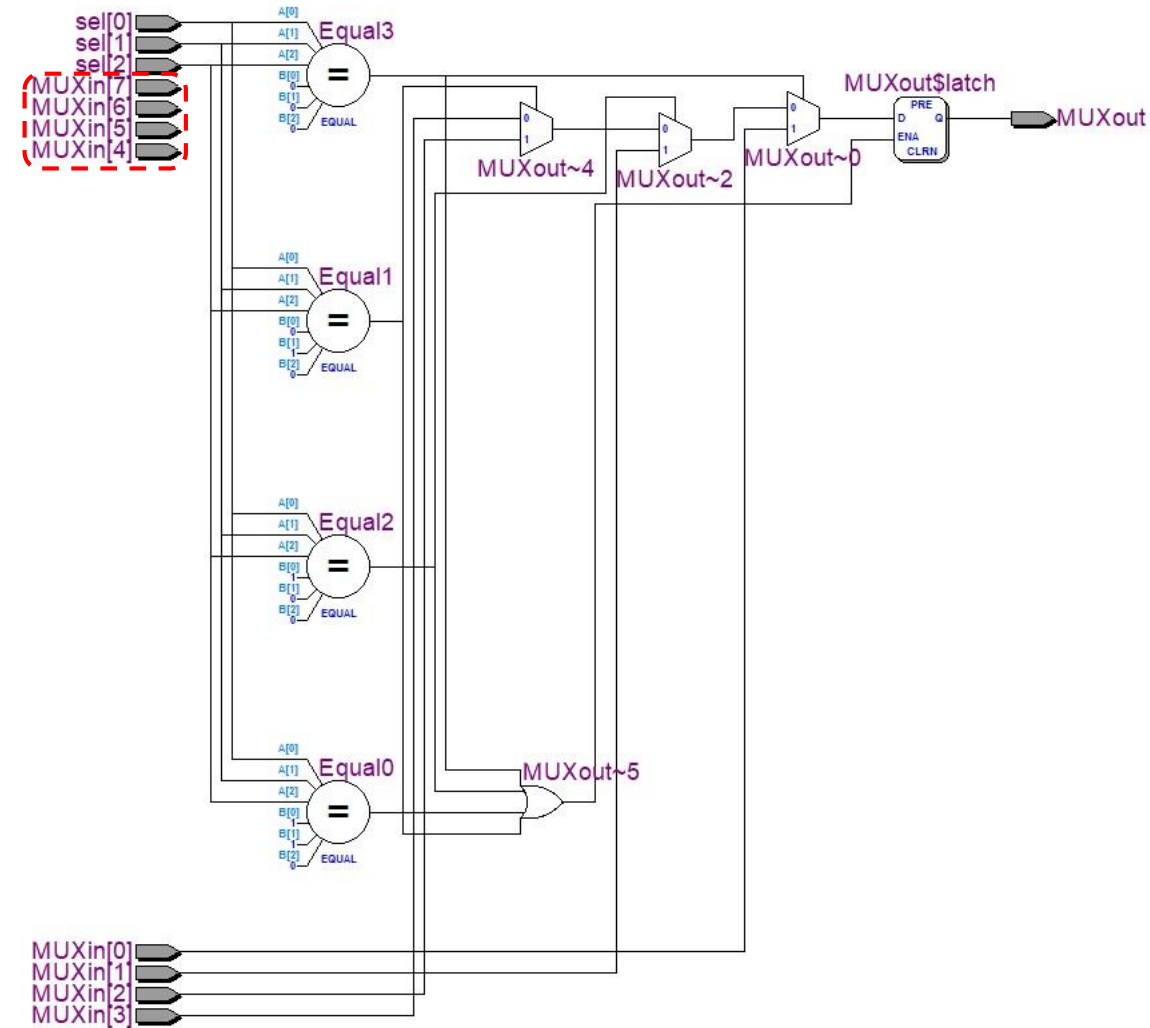

Conditional signal assignment (tri-state)

 
- **Example 3:**

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
-----  
ENTITY tri_state IS  
    PORT ( ena: IN STD_LOGIC;  
          input: IN STD_LOGIC_VECTOR (7 DOWNT0 0);  
          output: OUT STD_LOGIC_VECTOR (7 DOWNT0 0));  
END tri_state;  
-----  
ARCHITECTURE tri_state OF tri_state IS  
BEGIN  
    output <= input WHEN (ena='0') ELSE  
                (OTHERS => 'Z');  
END tri_state;
```



D latch using WHEN statement
 
```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
-----  
ENTITY D_latch IS  
    PORT (d, clk: IN STD_LOGIC;  
          q: BUFFER STD_LOGIC) ;  
END D_latch;  
-----  
ARCHITECTURE rtl OF D_latch IS  
BEGIN  
  
    q <= d when clk='1' else q;  
  
END rtl;
```




Selected signal assignment (mux as a True Table)

- Syntax:

```
WITH expression SELECT  
    signal_name <= assignment WHEN condition1 ,  
                                assignment WHEN condition2 ,  
                                ....  
                                ....  
                                assignment WHEN OTHERS ;
```

 - Example 1:

```
WITH sel SELECT  
    q <= a WHEN "00" ,  
        b WHEN "01" ,  
        c WHEN "10" ,  
        d WHEN OTHERS ;
```



Selected signal assignment (mux as a True Table)

Example 2:


```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

-----

ENTITY encoder IS
    PORT ( x: IN STD_LOGIC_VECTOR (7 DOWNTO 0);
          y: OUT STD_LOGIC_VECTOR (2 DOWNTO 0));
END encoder;

-----

ARCHITECTURE encoder2 OF encoder IS
BEGIN
    WITH x SELECT
        y <= "000" WHEN "00000001",
              "001" WHEN "00000010",
              "010" WHEN "00000100",
              "011" WHEN "00001000",
              "100" WHEN "00010000",
              "101" WHEN "00100000",
              "110" WHEN "01000000",
              "111" WHEN "10000000",
              "ZZZ" WHEN OTHERS;
END encoder2;
```

 

unaffected value using in With-Select statement

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;


-----
ENTITY mux3_8 IS
    GENERIC (n : INTEGER := 8;
             k : integer := 3 -- k=log2(n)
            );

    PORT (MUXIn:  IN STD_LOGIC_VECTOR(n-1 downto 0);
          sel:    IN STD_LOGIC_VECTOR(k-1 downto 0);
          MUXout: OUT STD_LOGIC);
END mux3_8;

-----
ARCHITECTURE rtl OF mux3_8 IS
BEGIN

    with sel(2 downto 0) select -- sel must be static
        MUXout <= MUXIn(0)  when "000",
                  MUXIn(1)  when "001",
                  MUXIn(2)  when "010",
                  MUXIn(3)  when "011",
                  unaffected when others; -- when others

END rtl;
```

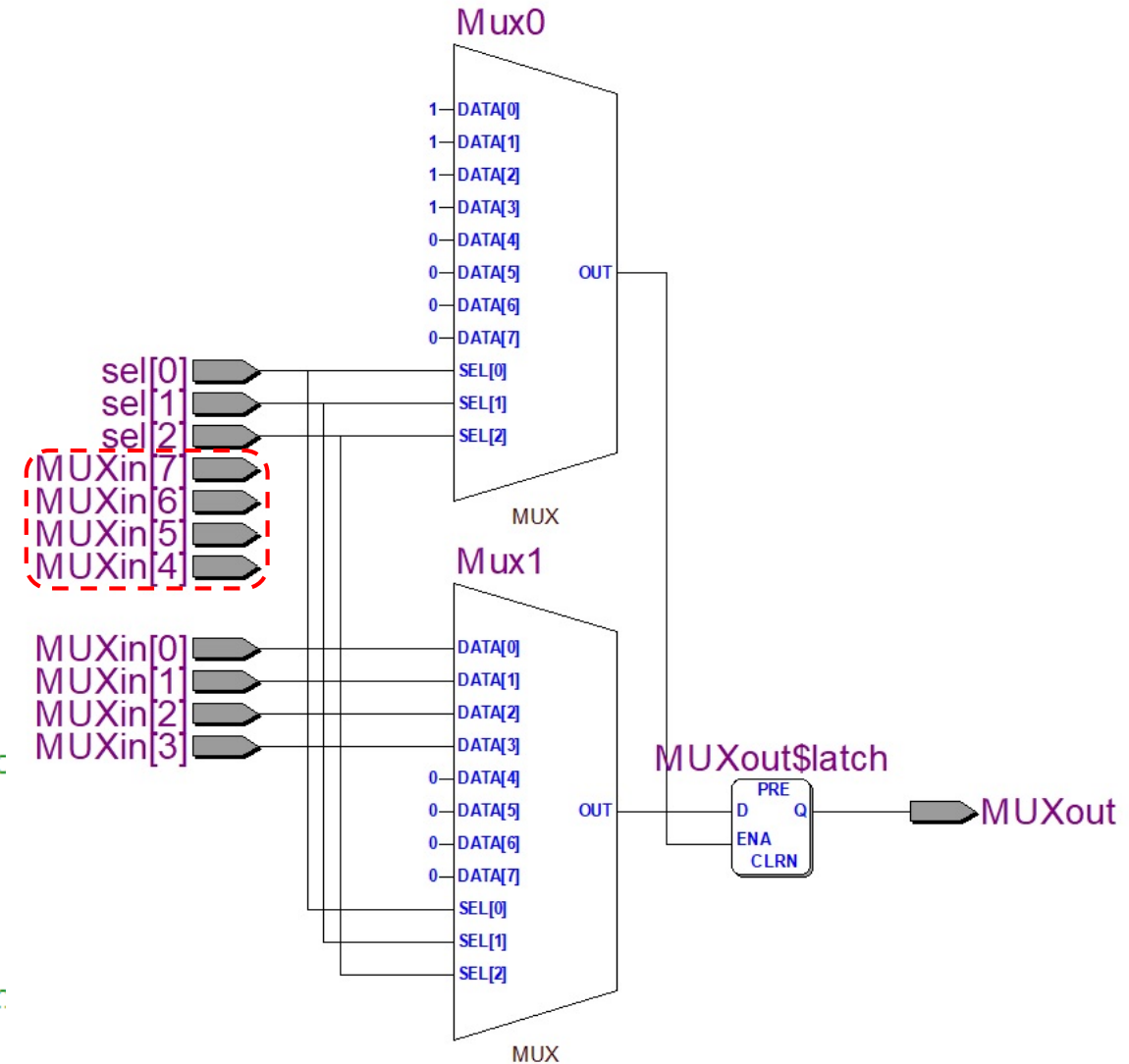

Generate

- **GENERATE** is another concurrent statement. *It allows a section of concurrent code to be repeated a number of times*, thus creating several instances of the same assignments.
- **GENERATE** statement must be labeled.
- **Formula 1 - FOR / GENERATE:**

```
label : FOR identifier IN range GENERATE  
        concurrent statements;  
END GENERATE;
```

Notes:

- the identifier range must be static.
- Be aware of avoiding from overlap assignments (multiple driven), **causes compilation error.**

FOR / GENERATE – multiple driven

- Example 1:

```
wrong: FOR i IN 0 TO 7 GENERATE  
    accum <="11111111" WHEN (a(i) AND b(i))='1' ELSE "00000000";  
END GENERATE;
```

- Example 2:

```
wrong: For i IN 0 to 7 GENERATE  
    accum <= accum + 1 WHEN x(i)='1' ELSE 0;  
END GENERATE;
```

Generate

- Formula 2 - IF / GENERATE :

```
label : IF condition GENERATE  
        concurrent statements;  
END GENERATE;
```

- Formula 3 - IF / GENERATE and FOR / GENERATE can be combined:

```
label1: IF condition GENERATE  
        .....  
        label2: FOR identifier IN range GENERATE  
                concurrent assignments;  
        END GENERATE;  
        .....  
END GENERATE;
```

```
label1: FOR identifier IN range GENERATE  
        .....  
        label2: IF condition GENERATE  
                concurrent assignments;  
        END GENERATE;  
        .....  
END GENERATE;
```

GENERATE - Vector Shifter Example

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

-----

ENTITY shifter IS
    PORT ( inp: IN STD_LOGIC_VECTOR (3 DOWNT0 0);
          sel: IN INTEGER RANGE 0 TO 4;
          outp: OUT STD_LOGIC_VECTOR (7 DOWNT0 0));
END shifter;

-----

ARCHITECTURE shifter OF shifter IS
    SUBTYPE vector IS STD_LOGIC_VECTOR (7 DOWNT0 0);
    TYPE matrix IS ARRAY (4 DOWNT0 0) OF vector;
    SIGNAL row: matrix;
BEGIN
    row(0) <= "0000" & inp;
    G1: FOR i IN 1 TO 4 GENERATE
        row(i) <= row(i-1) (6 DOWNT0 0) & '0';
    END GENERATE;
    outp <= row(sel); -- Mux inferred (pure logic of Memory structure)
END shifter;
```



For input:

inp="0011"

The result is:

row(0):	0 0 0 0 0 0 1 1	(decimal 3)
row(1):	0 0 0 0 0 1 1 0	(decimal 6)
row(2):	0 0 0 0 1 1 0 0	(decimal 12)
row(3):	0 0 0 1 1 0 0 0	(decimal 24)
row(4):	0 0 1 1 0 0 0 0	(decimal 48)

BLOCK

- There are two kinds of BLOCK statements:
Simple BLOCK and **Guarded BLOCK**.
- It allows a set of concurrent statements to be clustered into a **BLOCK**, with *the purpose of turning the overall code more readable and more manageable (helpful when dealing with long codes)*.
- Only concurrent statements can be written within a **BLOCK**.
- A **BLOCK** statement must be labeled.
- Declarations inside a **BLOCK** are seen by the **BLOCK** only.
- A **BLOCK** statement is local to the **ARCHITECTURE** where it's located.
- A **BLOCK** (simple or guarded) can be nested inside another **BLOCK**.

Simple BLOCK

- Syntax:

```
label1: BLOCK  
    [ generic; [ generic_map; ] ]  
    [ port; [ port_map; ] ]  
    [ block_declarations ]  
BEGIN  
    concurrent statements;  
END BLOCK label;
```

```
label1: BLOCK  
    [declarative part of top block]  
BEGIN  
    [concurrent statements of top block]  
    label2: BLOCK  
        [declarative part nested block]  
        BEGIN  
            (concurrent statements of nested block)  
        END BLOCK label2;  
    [more concurrent statements of top block]  
END BLOCK label1;
```

Guarded BLOCK

- A guarded BLOCK is a special kind of BLOCK, which includes an additional expression, called guard expression. A guarded statements in a guarded BLOCK is executed only when the guard expression is TRUE (unguarded statements will be executed anyway).
- Syntax:

```
label1: BLOCK (guard expression)
        [ generic; [ generic_map; ] ]
        [ port; [ port_map; ] ]
        [ block_declarations ]
BEGIN
        concurrent GUARDED statements;
END BLOCK label;
```


Guarded BLOCK – D Latch example

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
-----

ENTITY latch IS
    PORT (d, clk: IN STD_LOGIC;
          q: OUT STD_LOGIC);
END latch;
-----

ARCHITECTURE latch OF latch IS
BEGIN
    b1: BLOCK (clk='1')
    BEGIN
        q <= GUARDED d;
    END BLOCK b1;
END latch;
```

Guarded BLOCK – DFF example

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

-----

ENTITY dff IS
    PORT ( d, clk, rst: IN STD_LOGIC;
          q: OUT STD_LOGIC);
END dff;

-----

ARCHITECTURE dff OF dff IS
BEGIN
    b1: BLOCK (clk'EVENT AND clk='1')
    BEGIN
        q <= GUARDED '0' WHEN rst='1' ELSE d;
    END BLOCK b1;
END dff;
```