
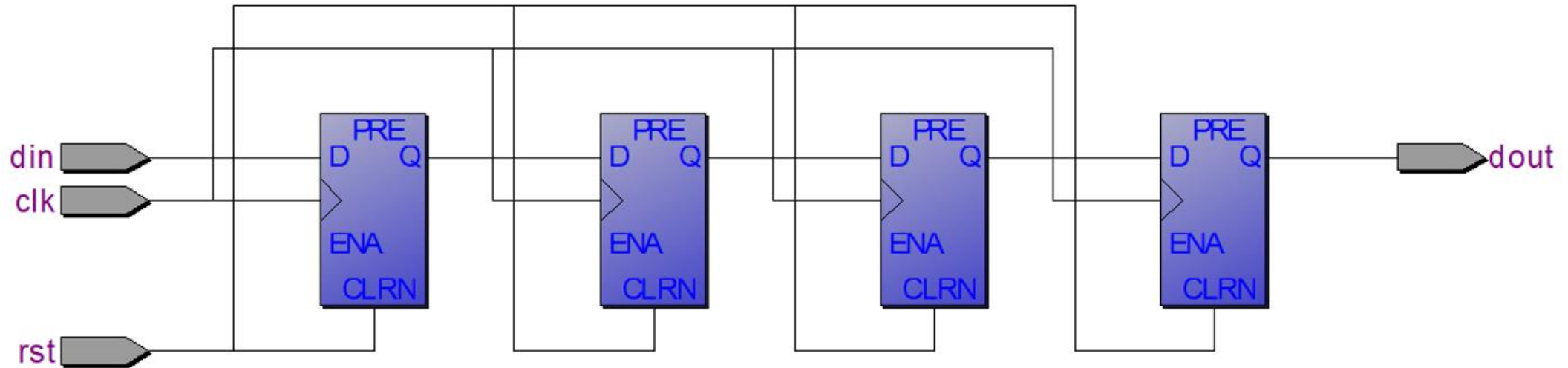


VHDL - Sequential PROCESS examples

©Hanan Ribo

4-stage shift register

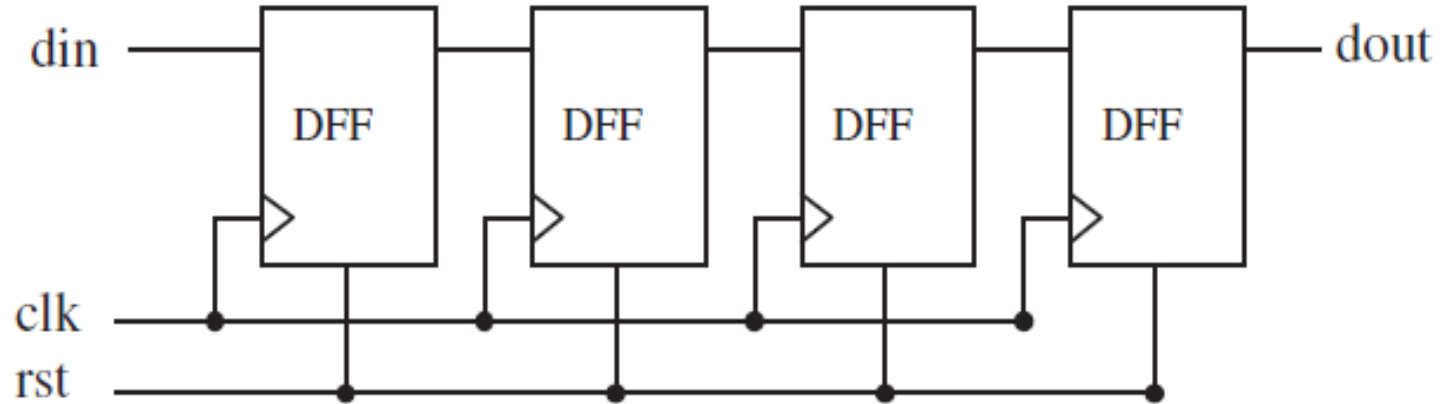We want to implement a Four Stages Shift-Register in different ways:



4-stage shift register (Behavioral approach)

```

library ieee;
use ieee.std_logic_1164.all;
-----


ENTITY ShiftRegisterVer1 IS
    GENERIC (n : integer := 3);
    PORT ( din, clk, rst: IN std_logic;
          dout: OUT std_logic);
    END ShiftRegisterVer1;
-----

ARCHITECTURE rtl OF ShiftRegisterVer1 IS
    SIGNAL internal: std_logic_vector (0 to n-1);
BEGIN
    PROCESS (clk, rst)
    BEGIN
        IF (rst='1') THEN
            internal <= (others => '0');
            dout <= '0';
        ELSIF (clk'EVENT and clk='1') THEN
            internal(0) <= din;
            for i in 0 to n-2 loop
                internal(i+1) <= internal(i);
            end loop;
            dout <= internal(n-1);
        END IF;
    END PROCESS;
END rtl;

```

Asynchronous part

Synchronous part

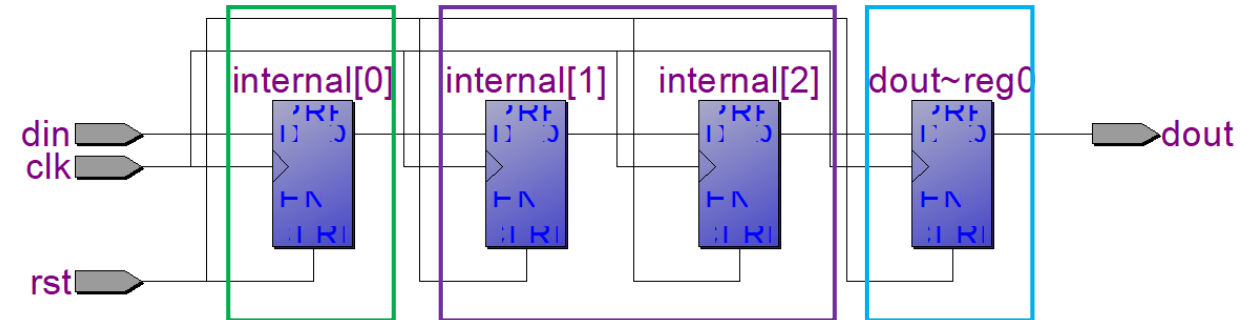

4-stage shift register (Structural approach)

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

-----

ENTITY dff IS
    PORT ( rst,clk,d: IN STD_LOGIC;
          q: OUT STD_LOGIC);
END dff;

-----


ARCHITECTURE rtl OF dff IS
BEGIN
    PROCESS (clk)
    BEGIN
        IF (rst='1') THEN
            q <= '0';
        ELSIF (clk'EVENT AND clk='1') THEN
            q <= d; -- generates a register
        END IF;
    END PROCESS;
END rtl;
    
```

```

ARCHITECTURE struct OF ShiftRegisterGenerate IS
    component dff
        PORT ( rst,clk,d: IN STD_LOGIC;
              q: OUT STD_LOGIC
            );
    end component;
    signal internal : std_logic_vector (0 to n-2);
BEGIN
    SHR: for i in 0 to n-1 generate
        first_dff: if i=0 generate
            dff1: dff port map(
                rst => rst, clk => clk, d => din,q =>internal(i));
            end generate;

        dffi: if (i>0 and i<n-1) generate
            dffi: dff port map(
                rst => rst, clk => clk, d => internal(i-1),q => internal(i));
            end generate;

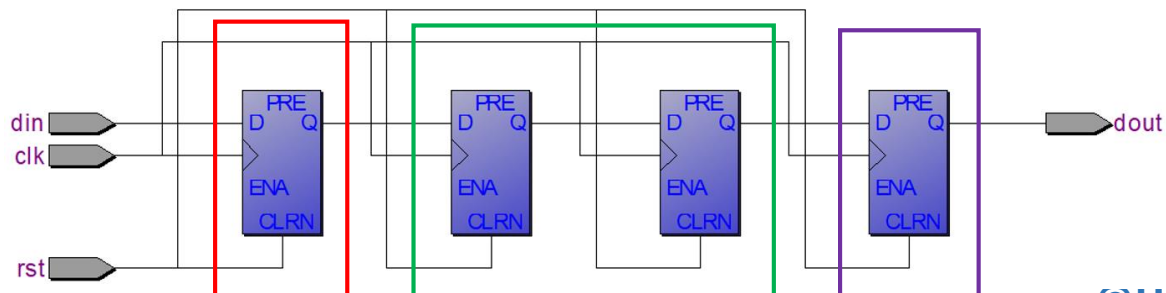        last_dff: if i=n-1 generate
            dff_n: dff port map(
                rst => rst, clk => clk, d => internal(i-2),q => dout);
            end generate;
    end generate;
END struct;
    
```



```

library ieee;
use ieee.std_logic_1164.all;

-----

ENTITY ShiftRegisterGenerate IS
    GENERIC (n : integer := 4);
    PORT (rst,clk,din : IN std_logic;
          dout: OUT std_logic
        );
END ShiftRegisterGenerate;
    
```

4-stage shift register (solution 3 - unrecommended)


```
library ieee;
use ieee.std_logic_1164.all;

-----

ENTITY ShiftRegisterVer4 IS
    PORT ( din, clk, rst: IN std_logic;
          dout: OUT std_logic);
END ShiftRegisterVer4;

-----

ARCHITECTURE rtl OF ShiftRegisterVer4 IS
BEGIN
    PROCESS (clk,rst)
        VARIABLE a, b, c: std_logic;
    BEGIN
        IF (rst='1') THEN
            a := '0';
            b := '0';
            c := '0';
            dout <= '0';
        ELSIF (clk'EVENT AND clk='1') THEN
            dout <= c;
            c := b;
            b := a;
            a := din;
        END IF;
    END PROCESS;
END rtl;
```

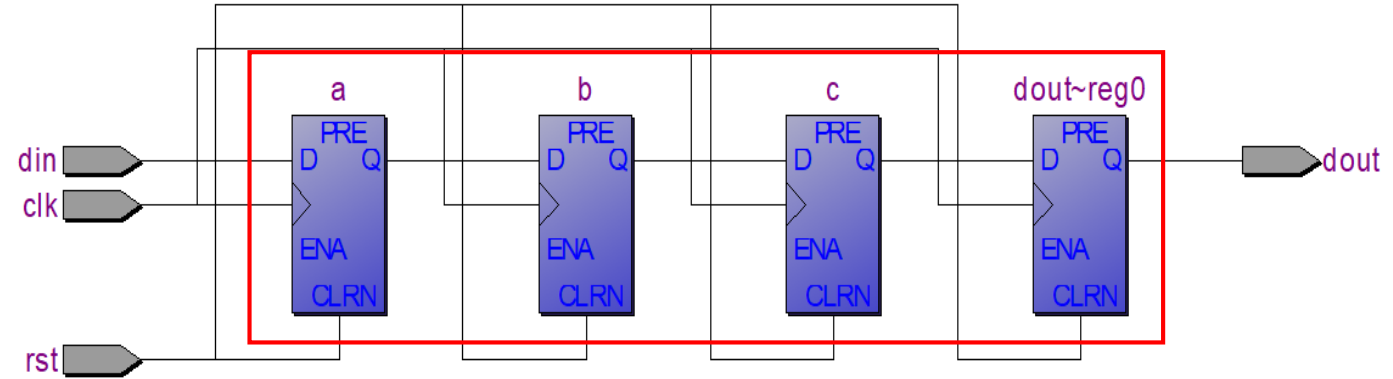

The way of using VARIABLES as memory elements, different from their original purpose

Frequency divider (version 1)

```

ENTITY freq_divider IS
    GENERIC(n : INTEGER := 8);
    PORT (    rst, clk : IN STD_LOGIC;
            out1, out2 : BUFFER STD_LOGIC);
END freq_divider;

-----

ARCHITECTURE rtl OF freq_divider IS
    SIGNAL count1 : INTEGER RANGE 0 TO n-1;
BEGIN
    PROCESS (clk)
        VARIABLE count2 : INTEGER RANGE 0 TO n-1 ;
    BEGIN
        IF (rst='1') THEN
            out1<='0';
            out2<='0';
        ELSIF (clk'EVENT AND clk='1') THEN
            count1 <= count1 + 1;
            count2 := count2 + 1;

            IF (count1 = 3 ) THEN
                out1 <= NOT out1;
                count1 <= 0;
            END IF;

            IF (count2 = 3 ) THEN
                out2 <= NOT out2;
                count2 := 0;
            END IF;
        END IF;
    END PROCESS;
END rtl;
    
```


Out1
combinational
logic

Out2
combinational
logic


Count1
combinational
logic

$f_{clk}/8$


$f_{clk}/6$

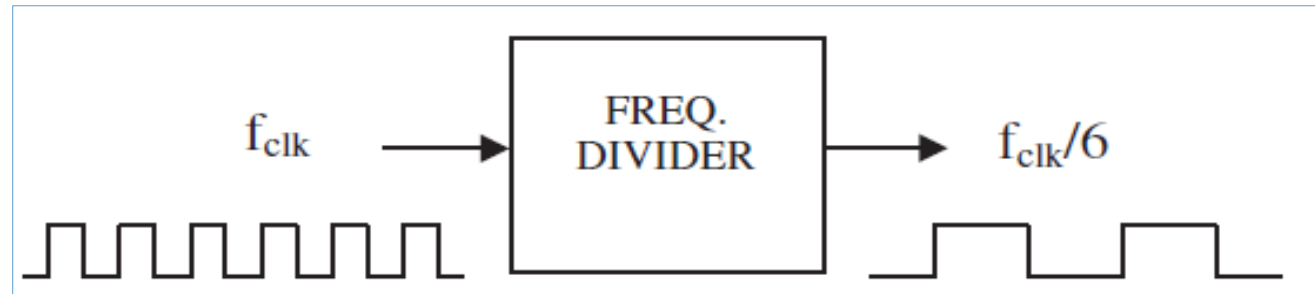


Simulation using ideal FFs

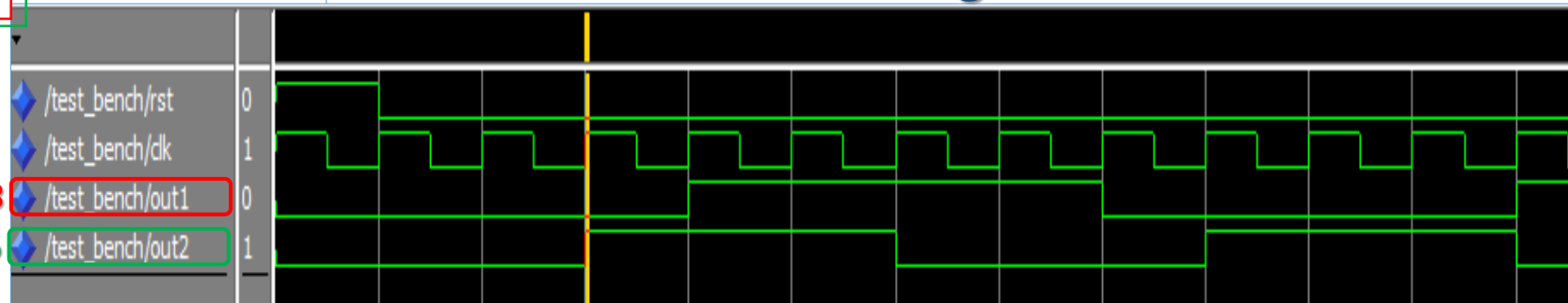

Frequency divider (version 1)

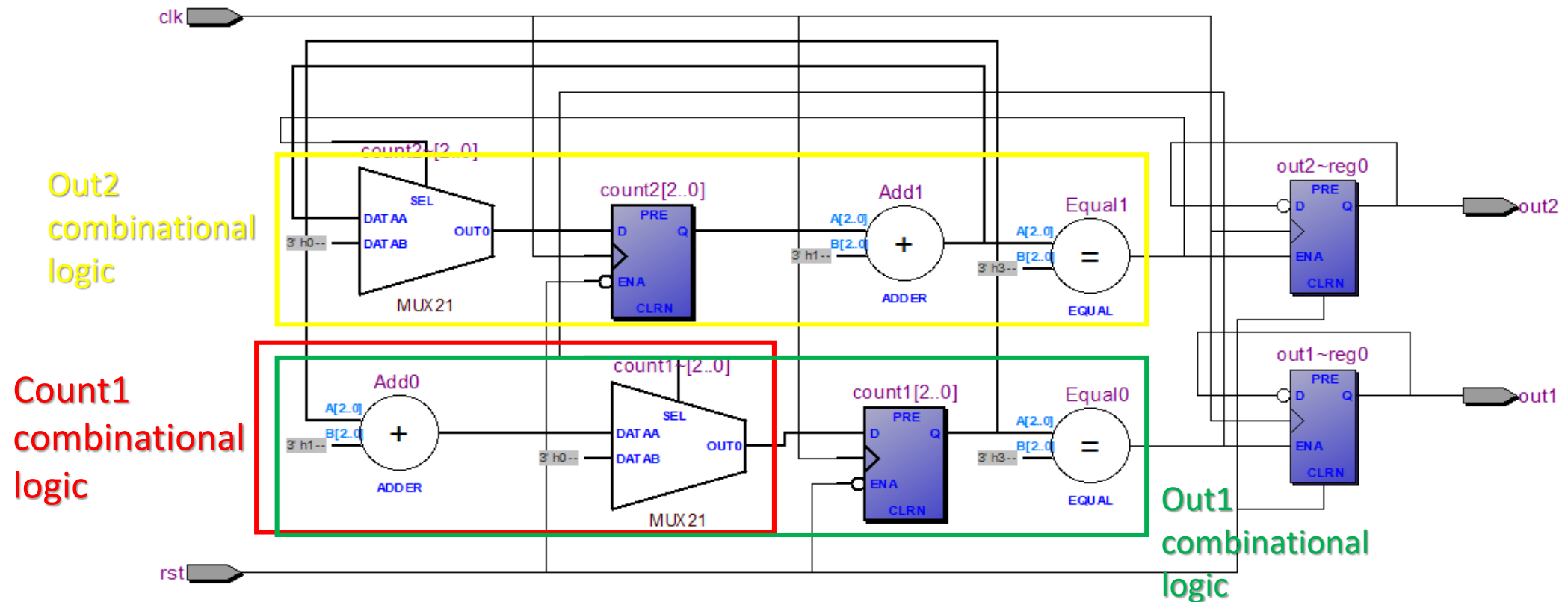

Using Signal TAP

 

Frequency divider (version 2)

```
library ieee;
use ieee.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;

entity freq_divider is
    GENERIC (n : INTEGER := 2 ; m : INTEGER := 1 );
    port (rst,clk : in std_logic;
          out1,out2 : out std_logic);
end freq_divider;
-----
architecture rtl of freq_divider is
    signal q_int : std_logic_vector (31 downto 0);
begin
    process (clk,rst)
    begin
        if(rst='1') then
            q_int <= (others => '0');
        elsif (rising_edge(clk)) then
            q_int <= q_int + 1;
        end if;
    end process;
    out1 <= q_int(n);  $f_{clk}/8$ 
    out2 <= q_int(m);  $f_{clk}/4$ 
end rtl;
```


Frequency divider (version 2)

