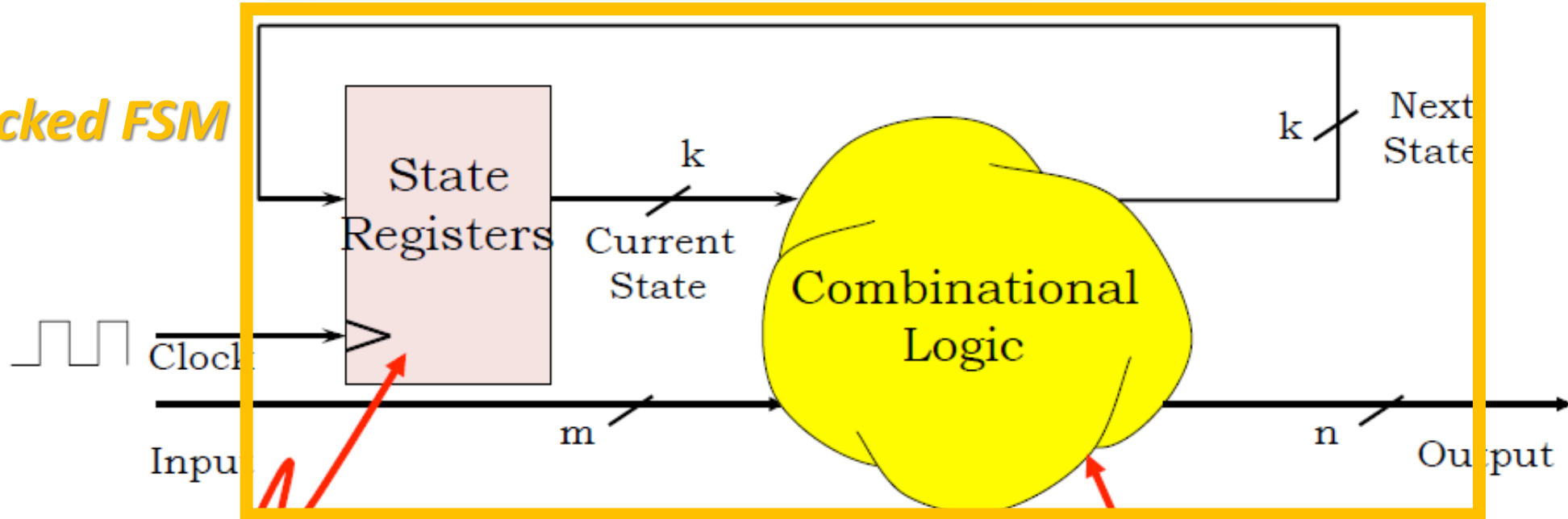


Synchronous FSM (Finite State Machine) Rehearsal

©Hanan Ribo

Synchronous FSM definition


Clocked FSM



- Engineered cycles
- Works only if dynamic discipline obeyed
- Remembers k bits for a total of 2^k unique combinations

- Acyclic graph
- Obeys static discipline
- Can be exhaustively enumerated by a truth table of 2^{k+m} rows and $k+n$ output columns



Synchronous FSM Abstraction

 


A FINITE STATE MACHINE has

- k STATES: $S_1 \dots S_k$ (one is “initial” state)
- m INPUTS: $I_1 \dots I_m$
- n OUTPUTS: $O_1 \dots O_n$
- Transition Rules: $s'(s, I)$ for each state s and input I
- Output Rules: $\text{Out}(s)$ or $\text{Out}(s, I)$ for each state s and input I

 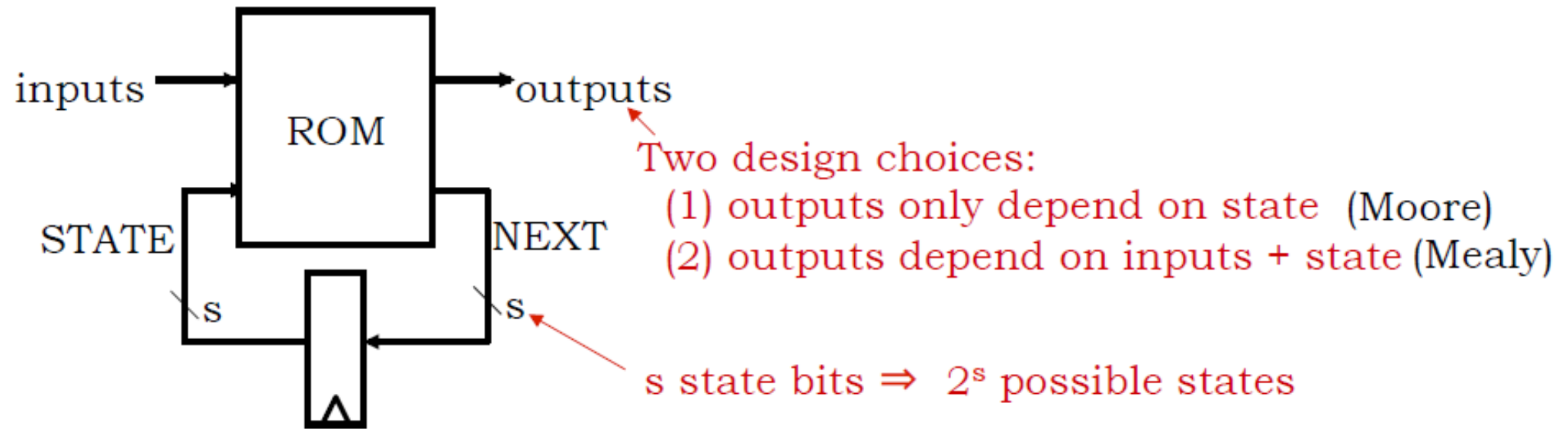Synchronous FSM - Discrete State, Discrete Time




Synchronous FSM - Initialization

 


Mealy vs. Moore Machines


Moore

 

input=(x,y)
output=(r,s,t)

 


Mealy

 

input=(x,y)
output=(r,s,t)


Mealy vs. Moore Machines

Moore

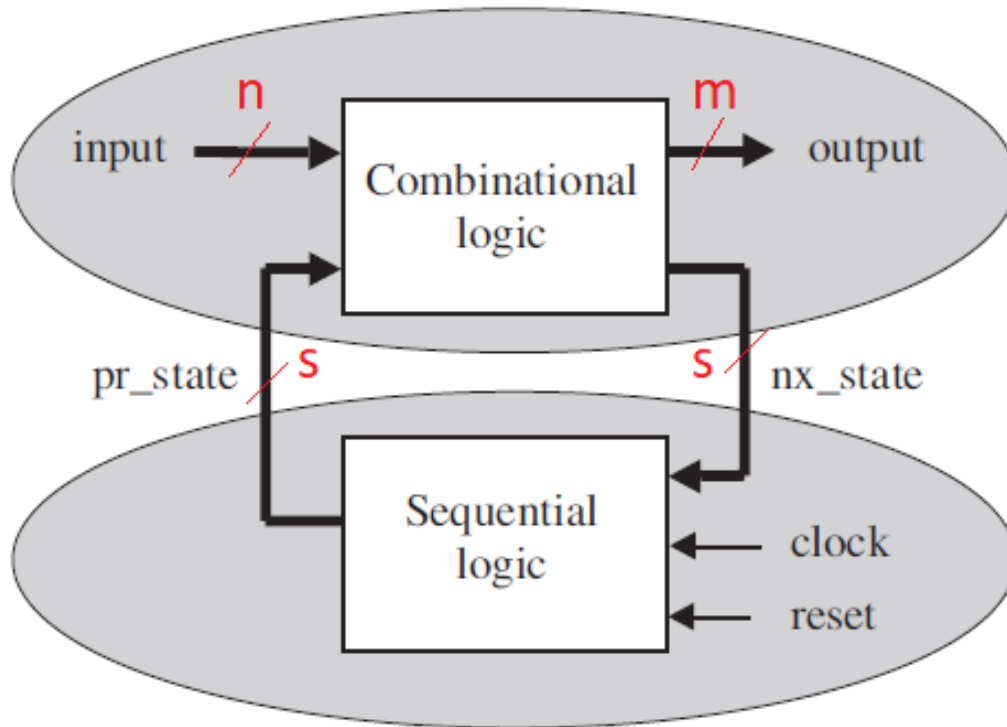

$$\text{output} = f(PS)$$
$$NS = g(\text{input}, PS)$$

Mealy

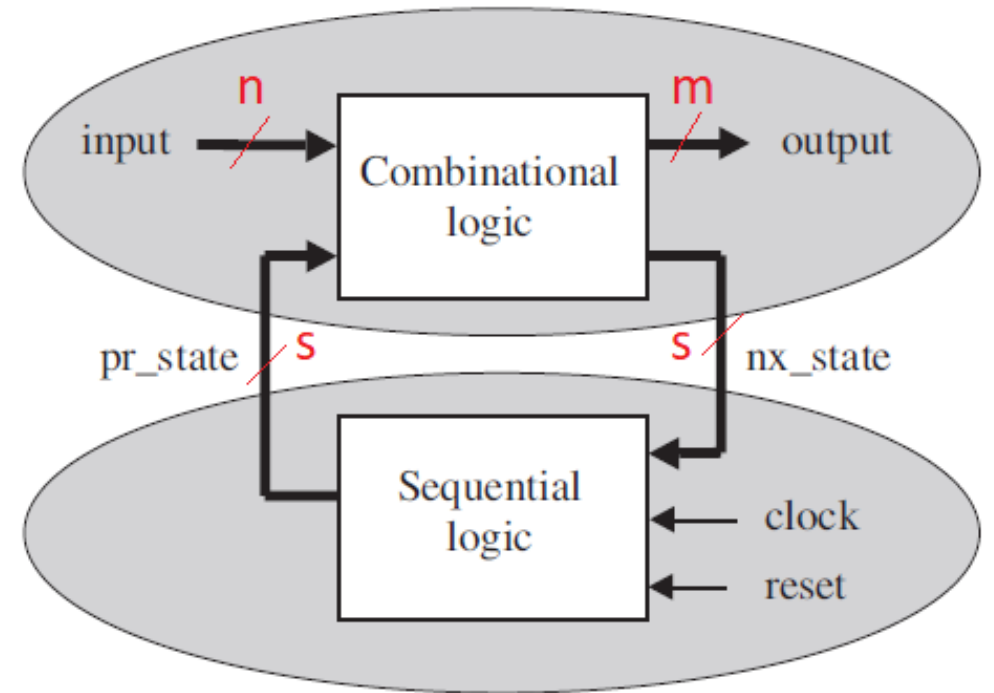



$$\text{output} = f(\text{input}, PS)$$
$$NS = g(\text{input}, PS)$$

FSM design Example




FSM design Example

You are required to design Up/Down modulo 4 counter with the next spec:

  - Input X uses as Up/Down selector (X='0' Up counter, X='1' Down counter).
- Output LED3,LED2 show the counter value.
- Output LED0 is set only on counter value transition from "00" to "11".
- Output LED1 is set only on counter value transition from "11" to "00".





FSM design Example

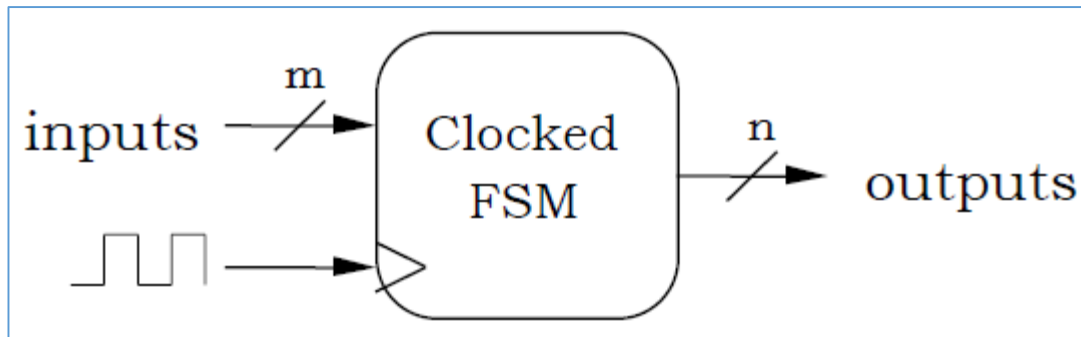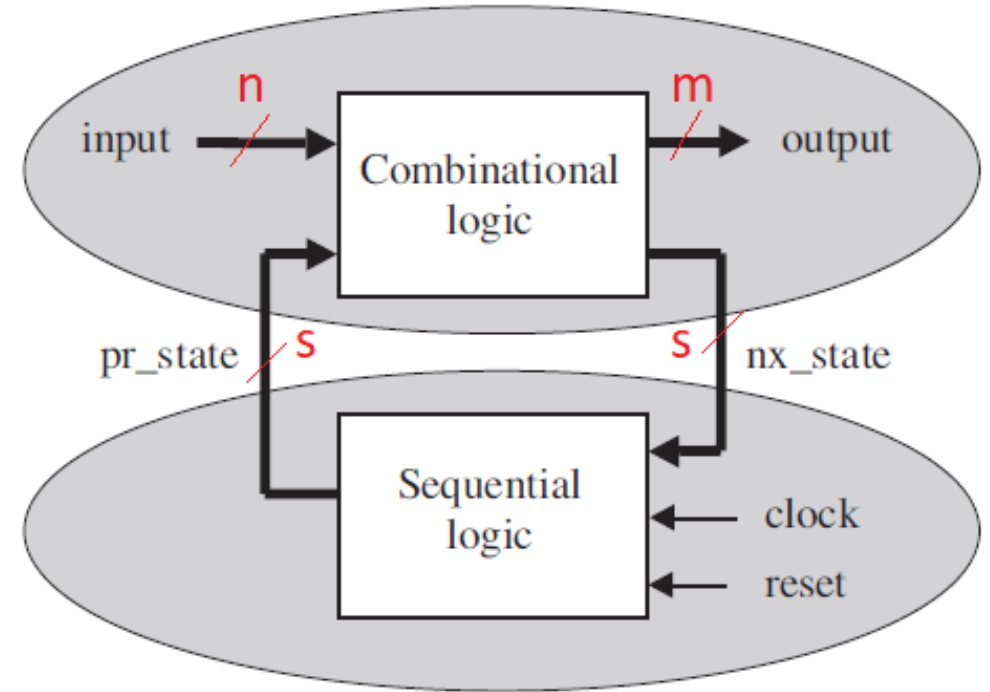 

$$\begin{aligned} (LED3, LED2) &= f(PS) \\ (LED1, LED0) &= f(X, PS) \\ NS &= g(X, PS) \end{aligned}$$

Phase 1 – Drawing of States Diagram

Symbolic Legend:

  

Thumb rule: The transitions condition from each state out are **disjoint** and **complement**.

For example:

State1 transitions condition out are: $x=1/00$, $x=0/00$ therefore $x \cdot \bar{x} = 0$ (**disjoint**) and $x + \bar{x} = 1$ (**complement**)

Phase 2 – Primitive Transitions Table

PS	Input X	X=0	X=1
State0		NS/LED1,LED0 = State1/00	NS/LED1,LED0 = State3/10
State1		NS/LED1,LED0 = State2/00	NS/LED1,LED0 = State0/00
State2		NS/LED1,LED0 = State3/00	NS/LED1,LED0 = State1/00
State3		NS/LED1,LED0 = State0/01	NS/LED1,LED0 = State2/00

$$PS \xrightarrow[\text{input } X]{\quad} NS / \text{Output}$$

This primitive table cannot be reduced (*recall that two states are identical iff their NS and Output are identical for the same input value*).


Phase 3 – States Encoding and Transitions table

State	Binary
State0	00
State1	01
State2	10
State3	11

$PS \triangleq \text{Present State} = (y_2, y_1)$

$NS \triangleq \text{Next State} = (Y_2, Y_1)$

Input X PS	X=0	X=1
State0	NS/LED1,LED0 = State1/00	NS/LED1,LED0 = State3/10
State1	NS/LED1,LED0 = State2/00	NS/LED1,LED0 = State0/00
State2	NS/LED1,LED0 = State3/00	NS/LED1,LED0 = State1/00
State3	NS/LED1,LED0 = State0/01	NS/LED1,LED0 = State2/00

 


X PS	X=0	X=1
00	01/00	11/10
01	10/00	00/00
10	11/00	01/00
11	00/01	10/00

Phase 4 – Implementation

Input X PS	X=0	X=1
State0	NS/LED1,LED0 = State1/00	NS/LED1,LED0 = State3/10
State1	NS/LED1,LED0 = State2/00	NS/LED1,LED0 = State0/00
State2	NS/LED1,LED0 = State3/00	NS/LED1,LED0 = State1/00
State3	NS/LED1,LED0 = State0/01	NS/LED1,LED0 = State2/00



X PS	X=0	X=1
00	01/00	11/10
01	10/00	00/00
10	11/00	01/00
11	00/01	10/00

 

		Y ₂ ,Y ₁ / LED1,LED0			
		x			
y ₂ ,y ₁		00	01	11	10
		0	2	6	4
0		01/00	10/00	00/01	11/00
1		11/10	00/00	10/00	01/00
		1	3	7	5

$PS \triangleq \text{Present State} = (y_2, y_1)$

$NS \triangleq \text{Next State} = (Y_2, Y_1)$

Phase 4 – Implementation

$PS \triangleq (y_2, y_1)$
 $NS \triangleq (Y_2, Y_1)$

		Y2 Y1 LED1 LED0			
x	y2,y1	00	01	11	10
	0	0 01/00	2 10/00	6 00/01	4 11/00
	1	1 11/10	3 00/00	7 10/00	5 01/00

$LED0 = y_2 \cdot y_1 \cdot \bar{x}$

		00	01	11	10
x	y2,y1	0 0	2 0	6 1	4 0
	1	1 0	3 0	7 0	5 0

$Y_2 = x \oplus y_2 \oplus y_1$

		00	01	11	10
x	y2,y1	0 0	2 1	6 0	4 1
	1	1 1	3 0	7 1	5 0

$LED1 = \bar{y}_2 \cdot \bar{y}_1 \cdot x$

		00	01	11	10
x	y2,y1	0 0	2 0	6 0	4 0
	1	1 1	3 0	7 0	5 0

$Y_1 = \bar{y}_1$

		00	01	11	10
x	y2,y1	0 1	2 0	6 0	4 1
	1	1 1	3 0	7 0	5 1

Phase 4 – Implementation

Tradeoff:

#DFFs

vs.

FANin and FANout size

Explanation:

Depending the States

Encoding Allocation (Binary

Encoding or Direct Encoding)

and

The target HW (LUT based
with low FANin but DFFs
abundantly as with FPGA or
the opposite with ASIC).

